
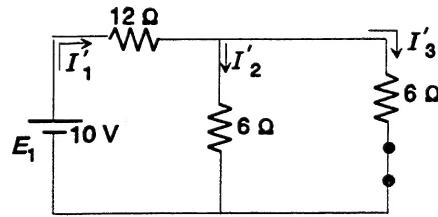


## CHAPTER 9 (Odd)

1. a.  $E_1$ :

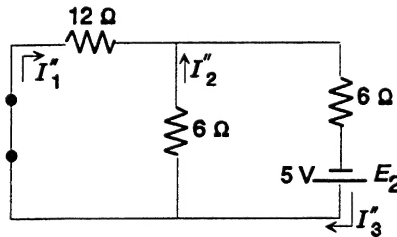

$E_2$ :



$$I'_1 = \frac{10 \text{ V}}{12 \Omega + 6 \Omega \parallel 6 \Omega} = \frac{10 \text{ V}}{12 \Omega + 3 \Omega} = \frac{2}{3} \text{ A}$$

$$I'_2 = I'_3 = \frac{I'_1}{2} = \frac{1}{3} \text{ A}$$

$$I''_3 = \frac{5 \text{ V}}{6 \Omega + 6 \Omega \parallel 12 \Omega} = \frac{5 \text{ V}}{6 \Omega + 4 \Omega} = \frac{1}{2} \text{ A}$$

$$I''_1 = \frac{6 \Omega (I''_3)}{6 \Omega + 12 \Omega} = \frac{1}{6} \text{ A}$$

$$I''_2 = \frac{12 \Omega (I''_3)}{12 \Omega + 6 \Omega} = \frac{1}{3} \text{ A}$$

$$I_1 = I'_1 + I''_1 = \frac{2}{3} \text{ A} + \frac{1}{6} \text{ A} = \frac{5}{6} \text{ A}$$

$$I_2 = I'_2 - I''_2 = \frac{1}{3} \text{ A} - \frac{1}{3} \text{ A} = 0 \text{ A}$$

$$I_3 = I'_3 + I''_3 = \frac{1}{3} \text{ A} + \frac{1}{2} \text{ A} = \frac{5}{6} \text{ A}$$


b.  $E_1$ :  $P'_1 = I'^2_1 R_1 = \left( \frac{2}{3} \text{ A} \right)^2 12 \Omega = 5.333 \text{ W}$

$E_2$ :  $P''_1 = I''^2_1 R_1 = \left( \frac{1}{6} \text{ A} \right)^2 12 \Omega = 0.333 \text{ W}$


c.  $P_1 = I^2_1 R_1 = \left( \frac{5}{6} \text{ A} \right)^2 12 \Omega = 8.333 \text{ W}$

d.  $P'_1 + P''_1 = 5.333 \text{ W} + 0.333 \text{ W} = 5.666 \text{ W} \neq 8.333 \text{ W} = P_1$

3. a.

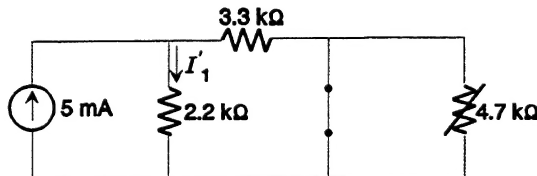


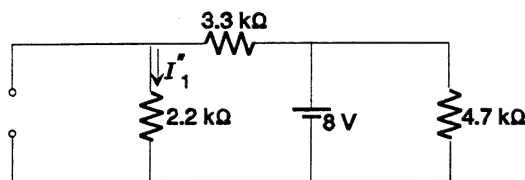
$$I_1 = \frac{3.3 \text{ k}\Omega (5 \text{ mA})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega} = \frac{16.5 \text{ mA}}{5.5} = 3 \text{ mA}$$



$$I''_1 = \frac{8 \text{ V}}{3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \frac{8 \text{ V}}{5.5 \text{ k}\Omega} = 1.4545 \text{ mA}$$



$$I_1 = I'_1 + I''_1 = 3 \text{ mA} + 1.4545 \text{ mA} = 4.4545 \text{ mA}$$

b.  $E_1$ :

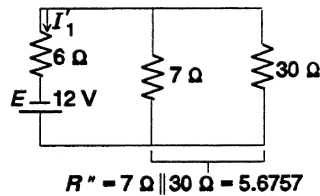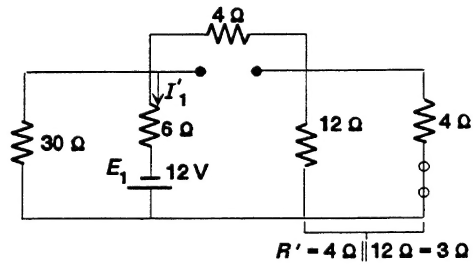

$$I'_1 = \frac{E_1}{R_T} = \frac{12\ \text{V}}{6\ \Omega + 5.6757\ \Omega} = 1.0278\ \text{A}$$


I:

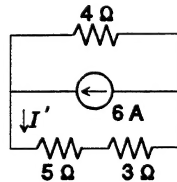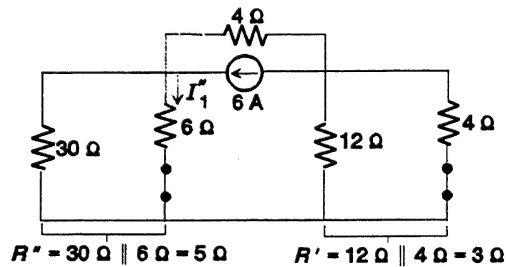

$$I' = \frac{4\ \Omega(6\ \text{A})}{4\ \Omega + 8\ \Omega} = 2\ \text{A}$$

$$I''_1 = \frac{30\ \Omega(2\ \text{A})}{30\ \Omega + 6\ \Omega} = 1.667\ \text{A}$$

$E_2$ :

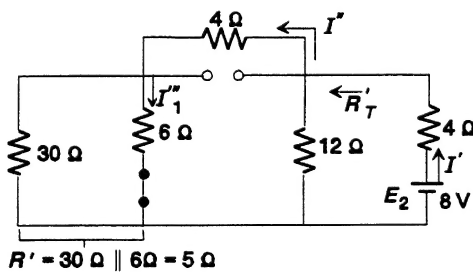

$$R'_T = 12\ \Omega \parallel (4\ \Omega + 5\ \Omega) = 12\ \Omega \parallel 9\ \Omega = 5.143\ \Omega$$

$$I' = \frac{E_2}{R_T} = \frac{8\ \text{V}}{4\ \Omega + 5.143\ \Omega} = 0.875\ \text{A}$$

$$I'' = \frac{12\ \Omega(I')}{12\ \Omega + 9\ \Omega} = \frac{12\ \Omega(0.875\ \text{A})}{21\ \Omega} = 0.5\ \text{A}$$

$$I'''_1 = \frac{30 \, \Omega (I''')}{30 \, \Omega + 6 \, \Omega} = \frac{30 \, \Omega (0.5 \, \text{A})}{36 \, \Omega} = 0.4167 \, \text{A}$$

$$I_1 = I_{R_1} = I'_1 + I''_1 + I'''_1 \\ = 1.0278 \, \text{A} + 1.667 \, \text{A} + 0.4167 \, \text{A} = 3.11 \, \text{A}$$

5. a.  $R_{Th} = R_3 + R_1 \parallel R_2 = 4 \, \Omega + 6 \, \Omega \parallel 3 \, \Omega = 4 \, \Omega + 2 \, \Omega = 6 \, \Omega$


$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{3 \, \Omega (18 \, \text{V})}{3 \, \Omega + 6 \, \Omega} = 6 \, \text{V}$$

b.  $I_1 = \frac{E_{Th}}{R_{Th} + R} = \frac{6 \, \text{V}}{6 \, \Omega + 2 \, \Omega} = 0.75 \, \text{A}$

$$I_2 = \frac{6 \, \text{V}}{6 \, \Omega + 30 \, \Omega} = 0.1667 \, \text{A}$$


$$I_3 = \frac{6 \, \text{V}}{6 \, \Omega + 100 \, \Omega} = 0.0566 \, \text{A}$$

7. (I):  $R_{Th}$ :

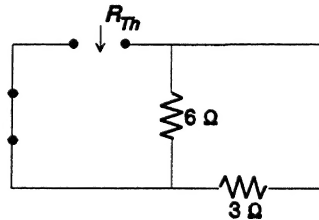

$$R_{Th} = 6 \, \Omega \parallel 3 \, \Omega = 2 \, \Omega$$


$E_{Th}$ :

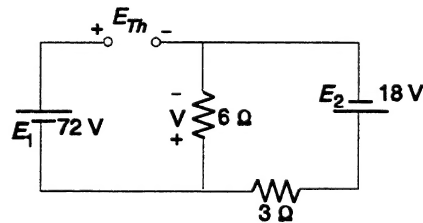

$$V = \frac{6 \, \Omega (18 \, \text{V})}{6 \, \Omega + 3 \, \Omega} = 12 \, \text{V}$$

$$E_{Th} = 72 \, \text{V} + V = 84 \, \text{V}$$


(II):  $R_{Th}$ :

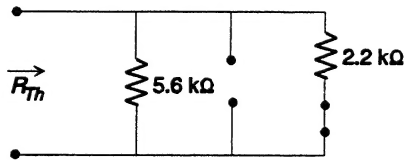

$$R_{Th} = 5.6 \, \text{k}\Omega \parallel 2.2 \, \text{k}\Omega = 1.579 \, \text{k}\Omega$$

$E_{Th}$ : Superposition:

I:

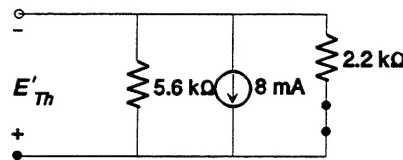


$$E'_{Th} = IR_T \\ = 8 \, \text{mA} (5.6 \, \text{k}\Omega \parallel 2.2 \, \text{k}\Omega) \\ = 8 \, \text{mA} (1.579 \, \text{k}\Omega) \\ = 12.636 \, \text{V}$$

$E$ :


$$E''_{Th} = \frac{5.6 \text{ k}\Omega (16 \text{ V})}{5.6 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 11.487 \text{ V}$$

$$E_{Th} = 11.487 \text{ V} - 12.636 \text{ V} = -1.149 \text{ V}$$


9. (I):  $R_{Th}$ :

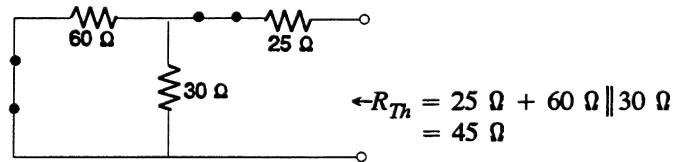


$E_{Th}$ :

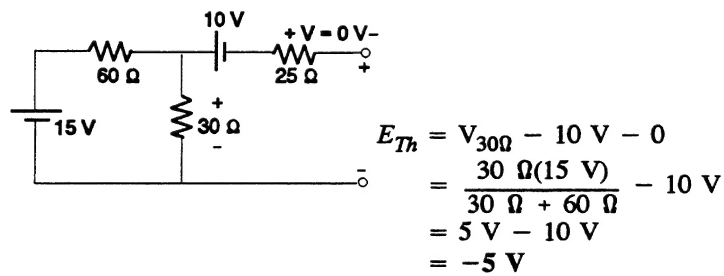


(II):  $R_{Th}$ :

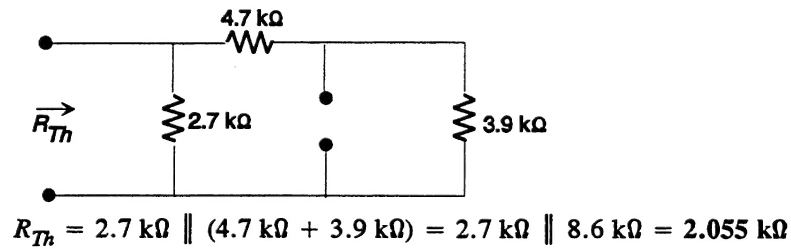

$E_{Th}$ :

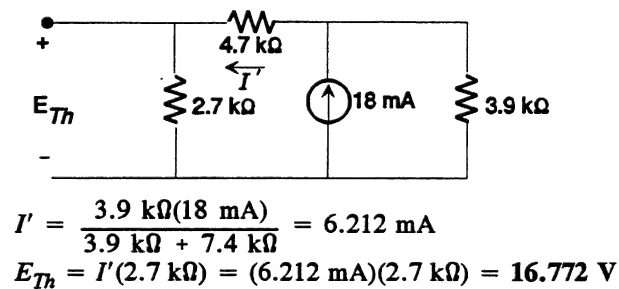

11.  $R_{Th}$ :

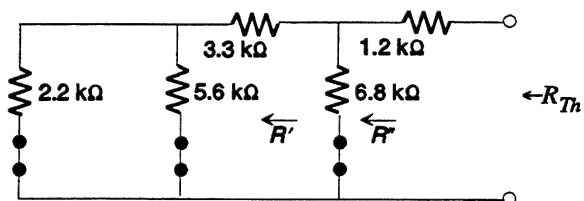

$$\begin{aligned} 2.2 \text{ k}\Omega \parallel 5.6 \text{ k}\Omega &= 1.579 \text{ k}\Omega \\ R' &= 1.579 \text{ k}\Omega + 3.3 \text{ k}\Omega \\ &= 4.879 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} R'' &= 4.879 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega = 2.841 \text{ k}\Omega \\ R_{Th} &= 1.2 \text{ k}\Omega + R'' = 1.2 \text{ k}\Omega + 2.841 \text{ k}\Omega = 4.041 \text{ k}\Omega \end{aligned}$$

$E_{Th}$ : Source conversions:

$$I_1 = \frac{22 \text{ V}}{2.2 \text{ k}\Omega} = 10 \text{ mA}, R_s = 2.2 \text{ k}\Omega$$

$$I_2 = \frac{12 \text{ V}}{5.6 \text{ k}\Omega} = 2.143 \text{ mA}, R_s = 5.6 \text{ k}\Omega$$


Combining parallel current sources:  $I'_T = I_1 - I_2 = 10 \text{ mA} - 2.143 \text{ mA} = 7.857 \text{ mA}$

$$2.2 \text{ k}\Omega \parallel 5.6 \text{ k}\Omega = 1.579 \text{ k}\Omega$$

Source conversion:

$$E = (7.857 \text{ mA})(1.579 \text{ k}\Omega) = 12.41 \text{ V}$$
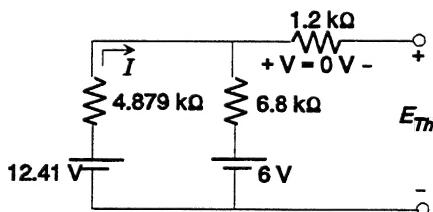
$$R' = R_s + 3.3 \text{ k}\Omega = 1.579 \text{ k}\Omega + 3.3 \text{ k}\Omega = 4.879 \text{ k}\Omega$$




$$I = \frac{12.41 \text{ V} - 6 \text{ V}}{4.879 \text{ k}\Omega + 6.8 \text{ k}\Omega} = \frac{6.41 \text{ V}}{11.679 \text{ k}\Omega} = 0.549 \text{ mA}$$

$$V_{6.8\text{k}\Omega} = I(6.8 \text{ k}\Omega) = (0.549 \text{ mA})(6.8 \text{ k}\Omega) = 3.733 \text{ V}$$


$$E_{Th} = 6 \text{ V} + V_{6.8\text{k}\Omega} = 6 \text{ V} + 3.733 \text{ V} = 9.733 \text{ V}$$

13. (I)  $R_N$ :



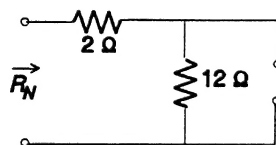


$$R_N = 2 \Omega + 12 \Omega = 14 \Omega$$



$I_N$ :

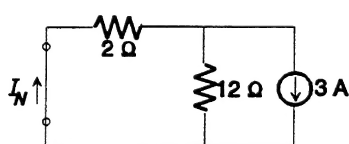

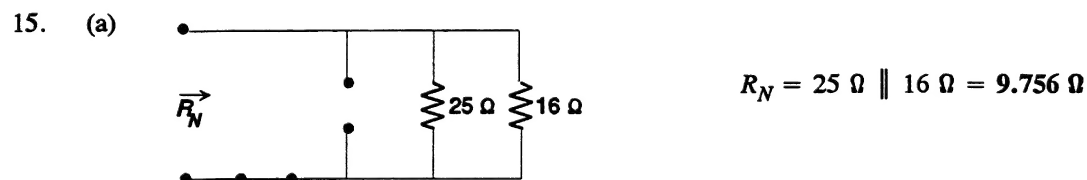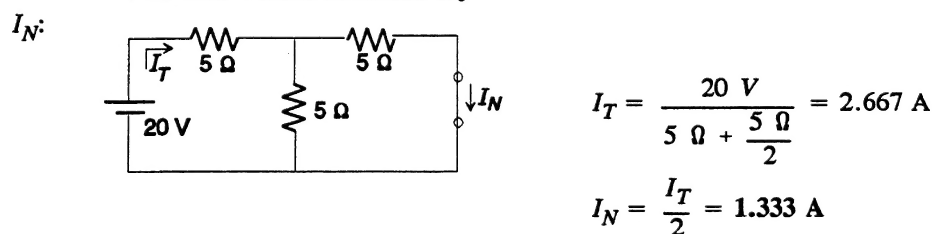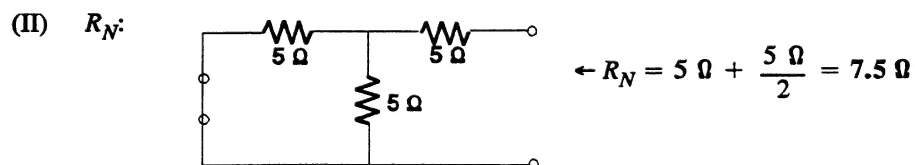
$$I_N = \frac{12 \Omega (3 \text{ A})}{12 \Omega + 2 \Omega} = 2.571 \text{ A}$$




$I_N$ : Superposition:

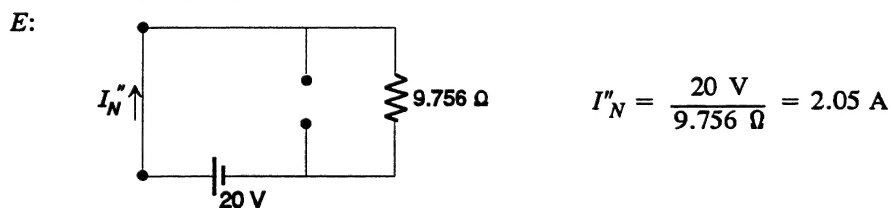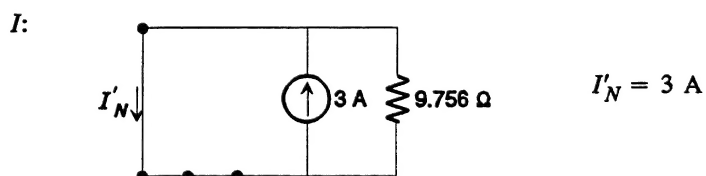
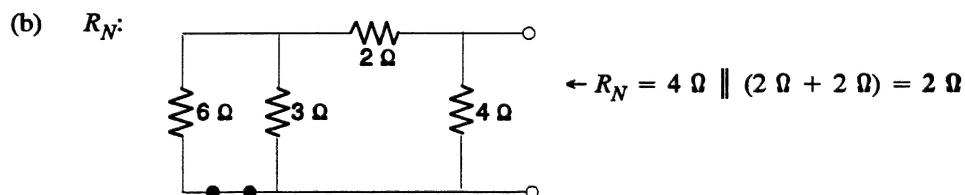
$$I_N = I'_N - I''_N = 3\ \text{A} - 2.05\ \text{A} = 0.95\ \text{A} \text{ (direction of } I'_N \text{)}$$



$I_N$ :

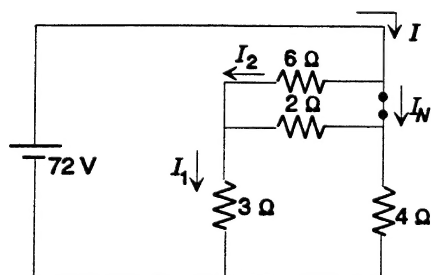

$$I = \frac{72 \text{ V}}{4 \Omega \parallel (3 \Omega + 6 \Omega \parallel 2 \Omega)}$$


$$= \frac{72 \text{ V}}{2.118 \Omega} \approx 34 \text{ A}$$

$$I_1 = \frac{4 \Omega(I)}{4 \Omega + 4.5 \Omega} = 16 \text{ A}$$

$$I_2 = \frac{2 \Omega(I_1)}{2 \Omega + 6 \Omega} = 4 \text{ A}$$

$$I_N = I - I_2 = 34 \text{ A} - 4 \text{ A} = 30 \text{ A}$$

17. (a)  $R_N$ :

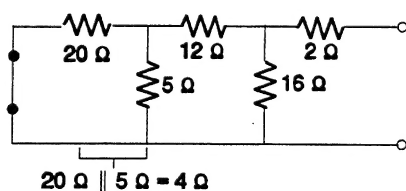


$$\leftarrow R_N = 2 \Omega + 16 \Omega \parallel (12 \Omega + 4 \Omega)$$

$$= 2 \Omega + 16 \Omega \parallel 16 \Omega$$

$$= 2 \Omega + 8 \Omega$$

$$= 10 \Omega$$

$I_N$ :

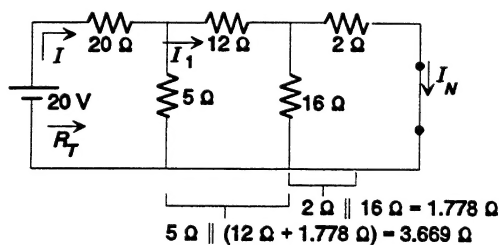


$$I = \frac{E}{R_T} = \frac{20 \text{ V}}{20 \Omega + 3.669 \Omega} = 0.845 \text{ A}$$

$$I_1 = \frac{5 \Omega(0.845 \text{ A})}{5 \Omega + 13.778 \Omega} = 0.225 \text{ A}$$

$$I_N = \frac{16 \Omega(0.225 \text{ A})}{16 \Omega + 2 \Omega} = 0.2 \text{ A}$$

(b)  $R_N$ :

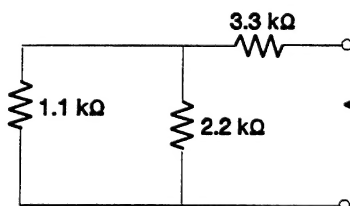


$$\leftarrow R_N = 3.3 \text{ k}\Omega + 1.1 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega$$

$$= 3.3 \text{ k}\Omega + 0.733 \text{ k}\Omega$$

$$= 4.033 \text{ k}\Omega$$

$I_N$ : Superposition:


$E_1$ :

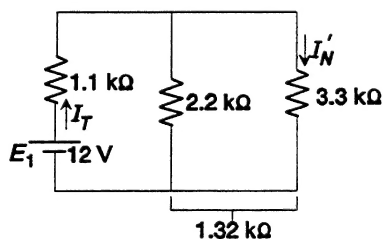

$$I_T = \frac{12 \text{ V}}{1.1 \text{ k}\Omega + 1.32 \text{ k}\Omega} = 4.959 \text{ mA}$$

$$I'_N = \frac{2.2 \text{ k}\Omega(4.959 \text{ mA})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega} = 1.984 \text{ mA}$$

$E_2$ :

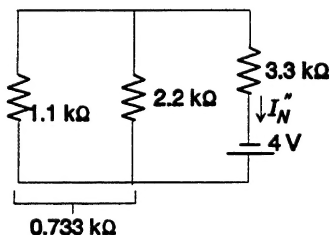


$$I''_N = \frac{4 \text{ V}}{3.3 \text{ k}\Omega + 0.733 \text{ k}\Omega} = 0.9918 \text{ mA}$$

$$I_N = I'_N + I''_N = 1.984 \text{ mA} + 0.9918 \text{ mA} = 2.9758 \text{ mA}$$

19. a. (I)  $R = R_{Th} = 14 \Omega$   
 (II)  $R = R_{Th} = 7.5 \Omega$
- b. (I)  $P_{\max} = E_{Th}^2/4R_{Th} = (36 \text{ V})^2/4(14 \Omega) = 23.14 \text{ W}$   
 (II)  $P_{\max} = E_{Th}^2/4R_{Th} = (10 \text{ V})^2/4(7.5 \Omega) = 3.33 \text{ W}$
21. a.  $R = R_{Th} = 9.756 \Omega$   
 b.  $R = R_{Th} = 2 \Omega$
- a.  $P_{\max} = E_{Th}^2/4R_{Th} = (9.268 \text{ V})^2/4(9.756 \Omega) = 2.20 \text{ W}$   
 b.  $P_{\max} = E_{Th}^2/4R_{Th} = (60 \text{ V})^2/4(2 \Omega) = 450 \text{ W}$

23. 
$$P_{\max} = \left( \frac{E_{Th}}{R_{Th} + R_4} \right)^2 R_4$$
  
 with  $R_1 = 0 \Omega$   $E_{Th}$  is a maximum and  $R_{Th}$  a minimum  
 $\therefore P_{\max}$  a maximum

25.

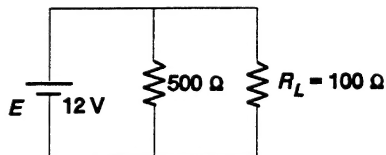

Since  $R_L$  fixed, maximum power to  $R_L$  when  $V_{R_L}$  a maximum as defined by  $P_L = \frac{V_{R_L}^2}{R_L}$

$$\therefore R = 500 \Omega \text{ and } P_{\max} = \frac{(12\text{V})^2}{100 \Omega} = 1.44 \text{ W}$$



$$27. \quad E_{eq} = \frac{-5 \text{ V}/2.2 \text{ k}\Omega + 20 \text{ V}/8.2 \text{ k}\Omega}{1/2.2 \text{ k}\Omega + 1/8.2 \text{ k}\Omega} = 0.2879 \text{ V}$$

$$R_{eq} = \frac{1}{1/2.2 \text{ k}\Omega + 1/8.2 \text{ k}\Omega} = 1.7346 \text{ k}\Omega$$

$$I_L = \frac{E_{eq}}{R_{eq} + R_L} = \frac{0.2879 \text{ V}}{1.7346 \text{ k}\Omega + 5.6 \text{ k}\Omega} = 39.3 \mu\text{A}$$

$$V_L = I_L R_L = (39.3 \mu\text{A})(5.6 \text{ k}\Omega) = 220 \text{ mV}$$

$$29. \quad I_{eq} = \frac{(4 \text{ A})(4.7 \Omega) + (1.6 \text{ A})(3.3 \Omega)}{4.7 \Omega + 3.3 \Omega} = \frac{18.8 \text{ V} + 5.28 \text{ V}}{8 \Omega} = 3.01 \text{ A}$$

$$R_{eq} = 4.7 \Omega + 3.3 \Omega = 8 \Omega$$




$$I_L = \frac{R_{eq}(I_{eq})}{R_{eq} + R_L} = \frac{8 \Omega(3.01 \text{ A})}{8 \Omega + 2.7 \Omega} = 2.25 \text{ A}$$

$$V_L = I_L R_L = (2.25 \text{ A})(2.7 \Omega) = 6.075 \text{ V}$$


$$31. \quad 15 \text{ k}\Omega \parallel (8 \text{ k}\Omega + 7 \text{ k}\Omega) = 15 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$V_{ab} = \frac{7.5 \text{ k}\Omega(60 \text{ V})}{7.5 \text{ k}\Omega + 2.5 \text{ k}\Omega} = 45 \text{ V}$$
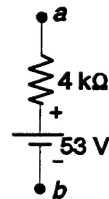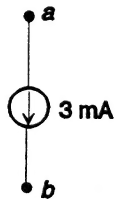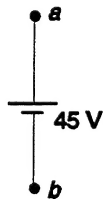
$$I_{ab} = \frac{45 \text{ V}}{15 \text{ k}\Omega} = 3 \text{ mA}$$



33.

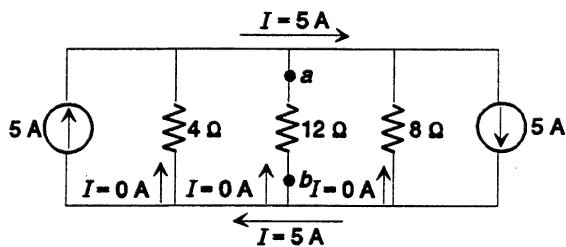


$$V_{ab} = 0 \text{ V (short)}$$

$$I_{ab} = 0 \text{ A (open)}$$

$R_2$  any resistive value

$\therefore R_2 = \text{short-circuit, open-circuit, any value}$


35. (a)

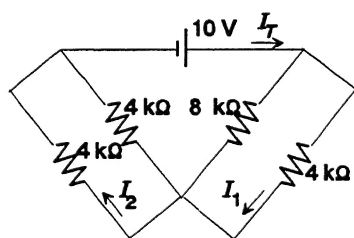

$$\begin{aligned}
 I_T &= \frac{10 \text{ V}}{4 \text{ k}\Omega \parallel 8 \text{ k}\Omega + 4 \text{ k}\Omega \parallel 4 \text{ k}\Omega} \\
 &= \frac{10 \text{ V}}{2.667 \text{ k}\Omega + 2 \text{ k}\Omega} \\
 &= \frac{10 \text{ V}}{4.667 \text{ k}\Omega} = 2.143 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 I_1 &= \frac{8 \text{ k}\Omega (I_T)}{8 \text{ k}\Omega + 4 \text{ k}\Omega} = 1.429 \text{ mA}, \quad I_2 = I_T/2 = 1.0715 \text{ mA} \\
 I &= I_1 - I_2 = 1.429 \text{ mA} - 1.0715 \text{ mA} = 0.357 \text{ mA}
 \end{aligned}$$

(b)

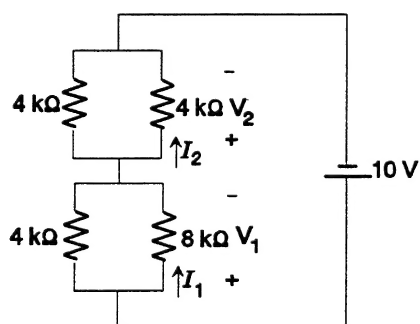

$$\begin{aligned}
 V_1 &= \frac{(8 \text{ k}\Omega \parallel 4 \text{ k}\Omega)(10 \text{ V})}{8 \text{ k}\Omega \parallel 4 \text{ k}\Omega + 4 \text{ k}\Omega \parallel 4 \text{ k}\Omega} \\
 &= 5.715 \text{ V}
 \end{aligned}$$

$$I_1 = \frac{V_1}{8 \text{ k}\Omega} = 0.714 \text{ mA}$$


$$\begin{aligned}
 V_2 &= E - V_1 = 10 \text{ V} - 5.715 \text{ V} \\
 &= 4.285 \text{ V}
 \end{aligned}$$

$$I_2 = \frac{V_2}{4 \text{ k}\Omega} = 1.071 \text{ mA}$$

$$\begin{aligned}
 I &= I_2 - I_1 = 1.071 \text{ mA} - 0.714 \text{ mA} \\
 &= 0.357 \text{ mA}
 \end{aligned}$$


## CHAPTER 9 (Even)

2. a.  $I$ :

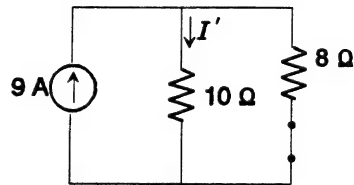

$$I' = \frac{8\ \Omega(9\ \text{A})}{8\ \Omega + 10\ \Omega} = 4\ \text{A}$$


$E$ :

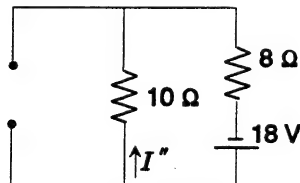

$$I'' = \frac{18\ \text{V}}{10\ \Omega + 8\ \Omega} = 1\ \text{A}$$

$$I(\text{dir. of } I') = I' - I'' = 4\ \text{A} - 1\ \text{A} = 3\ \text{A}$$

b.  $E_1$ :

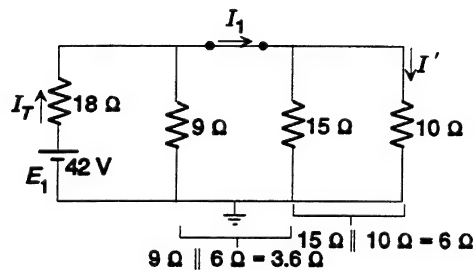


$$I_T = \frac{42\ \text{V}}{18\ \Omega + 3.6\ \Omega} = 1.944\ \text{A}$$

$$I_1 = \frac{9\ \Omega(I_T)}{9\ \Omega + 6\ \Omega} = \frac{9\ \Omega(1.944\ \text{A})}{15\ \Omega} = 1.1664\ \text{A}$$

$$I' = \frac{15\ \Omega(I_1)}{15\ \Omega + 10\ \Omega} = \frac{15\ \Omega(1.1664\ \text{A})}{25\ \Omega} = 0.7\ \text{A}$$

$E_2$ :

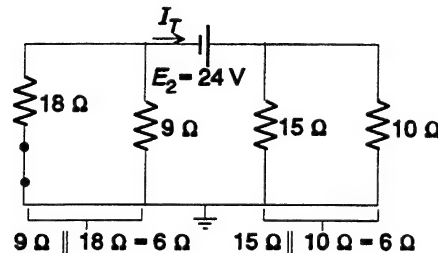


$$I_T = \frac{E_2}{R_T} = \frac{24\ \text{V}}{12\ \Omega} = 2\ \text{A}$$

$$I'' = \frac{15\ \Omega(I_T)}{15\ \Omega + 10\ \Omega} = 1.2\ \text{A}$$


$$I_{10\Omega} = I' + I'' = 0.7\ \text{A} + 1.2\ \text{A} = 1.9\ \text{A}$$

4.  $E$ :

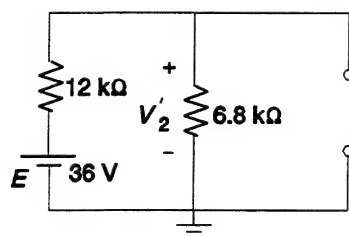

$$V_2' = \frac{6.8\ \text{k}\Omega(36\ \text{V})}{6.8\ \text{k}\Omega + 12\ \text{k}\Omega} = 13.02\ \text{V}$$

I:


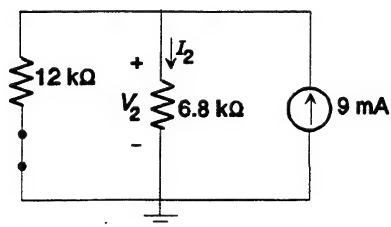


$$I_2 = \frac{12 \text{ k}\Omega (9 \text{ mA})}{12 \text{ k}\Omega + 6.8 \text{ k}\Omega} = 5.745 \text{ mA}$$

$$V''_2 = I_2 R_2 = (5.745 \text{ mA})(6.8 \text{ k}\Omega) = 39.06 \text{ V}$$

$$V_2 = V'_2 + V''_2 = 13.02 \text{ V} + 39.06 \text{ V} = 52.08 \text{ V}$$

6. (I) a.

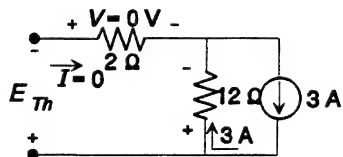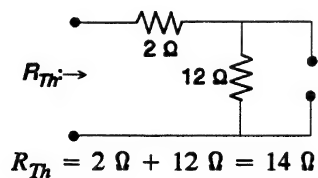



$$E_{Th} = IR = (3 \text{ A})(12 \Omega) = 36 \text{ V}$$

b.


$$R = 2 \Omega: P = \left[ \frac{E_{Th}}{R_{Th} + R} \right]^2 R = \left[ \frac{36 \text{ V}}{14 \Omega + 2 \Omega} \right]^2 2 \Omega = 10.125 \text{ W}$$

$$R = 100 \Omega: P = \left[ \frac{36 \text{ V}}{14 \Omega + 100 \Omega} \right]^2 100 \Omega = 9.9723 \text{ W}$$



(II) a.

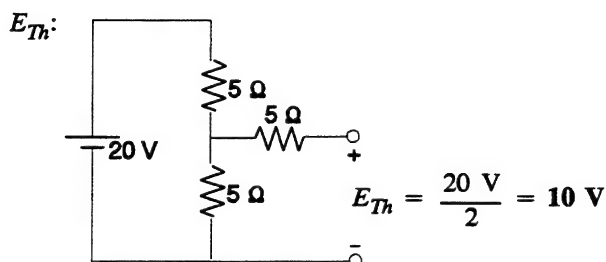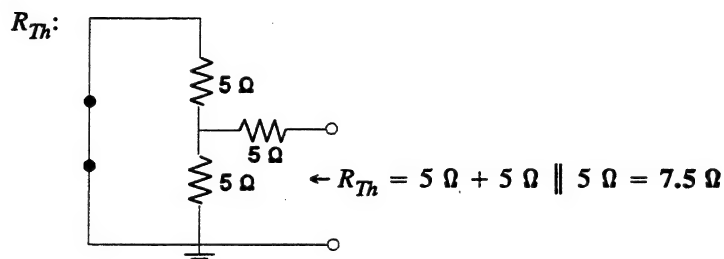


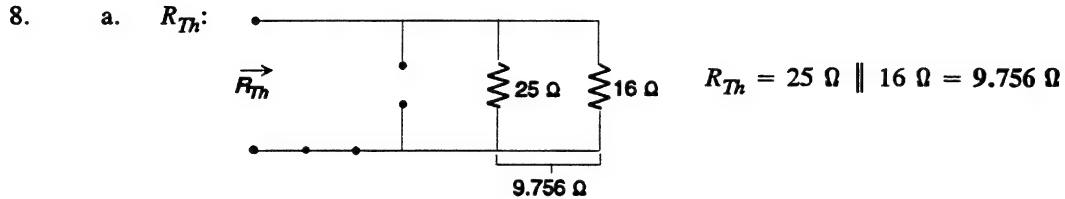
$$\begin{aligned} \text{b. } R = 2 \, \Omega: P &= \left( \frac{E_{Th}}{R_{Th} + R} \right)^2 R = \left( \frac{10 \, \text{V}}{7.5 \, \Omega + 2 \, \Omega} \right)^2 2 \, \Omega = 2.2161 \, \text{W} \\ R = 100 \, \Omega: P &= \left( \frac{10 \, \text{V}}{7.5 \, \Omega + 100 \, \Omega} \right)^2 100 \, \Omega = 0.8653 \, \text{W} \end{aligned}$$




$E_{Th}$ : Superposition:

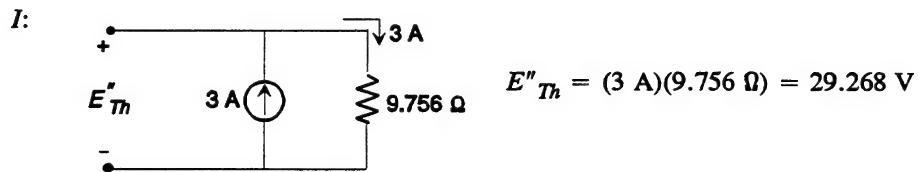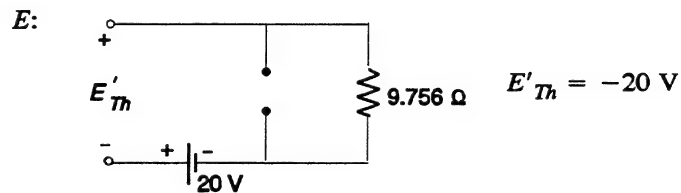

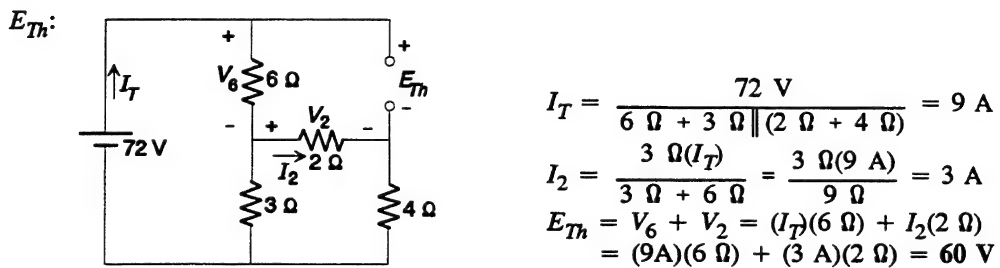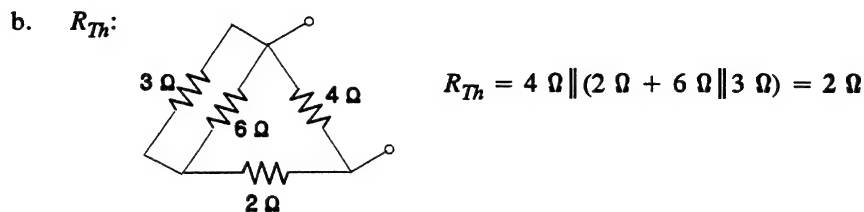
$$E_{Th} = E''_{Th} - E'_{Th} = 29.268 \, \text{V} - 20 \, \text{V} = 9.268 \, \text{V}$$



10. a.  $R_{Th}$ :

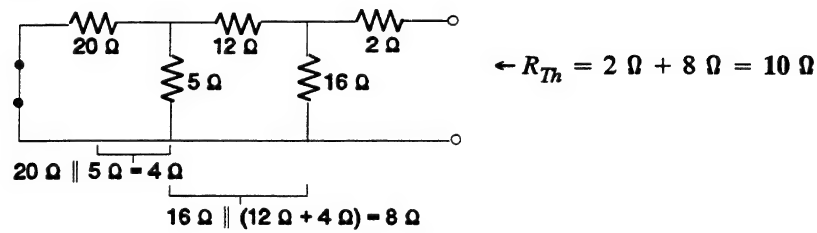

$E_{Th}$ :

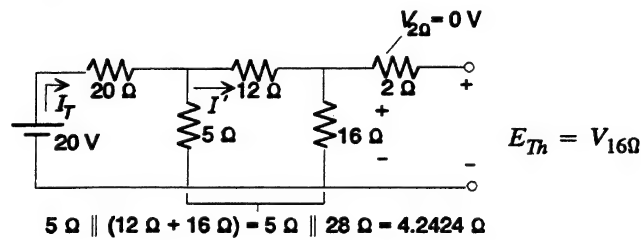


$$I_T = \frac{20\text{ V}}{20\ \Omega + 4.2424\ \Omega} = 0.825\text{ A}$$

$$I' = \frac{5\ \Omega(I_T)}{5\ \Omega + 28\ \Omega} = \frac{5\ \Omega(0.825\text{ A})}{33\ \Omega} = 0.125\text{ A}$$



$$E_{Th} = V_{16\Omega} = (I')(16\ \Omega) = (0.125\text{ A})(16\ \Omega) = 2\text{ V}$$

b.  $R_{Th}$ :

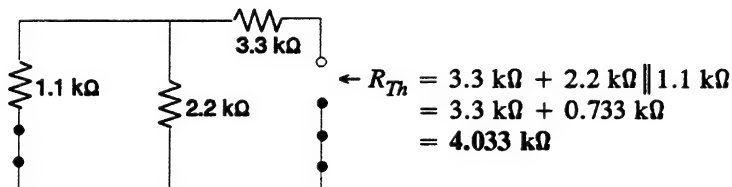


$E_{Th}$ : Superposition:

$E_1$ :

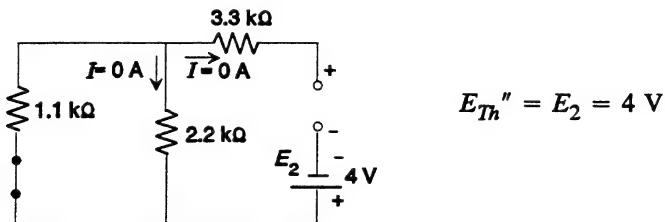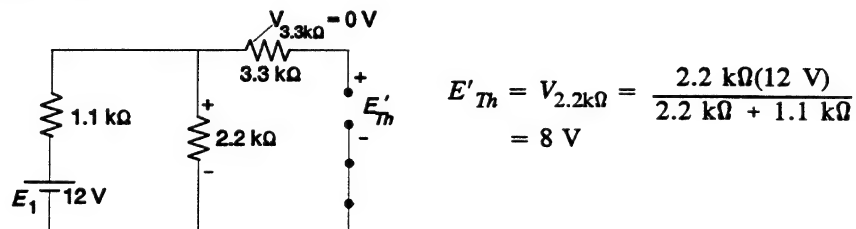


$$E_{Th} = E'_Th + E''_Th = 8\text{ V} + 4\text{ V} = 12\text{ V}$$

12. a.  $R_{Th}$ :

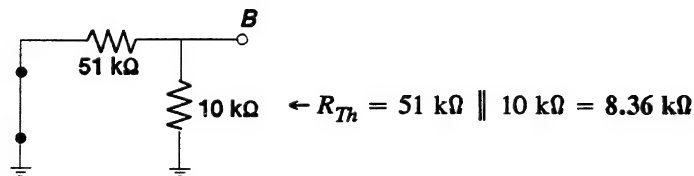


$E_{Th}$ :

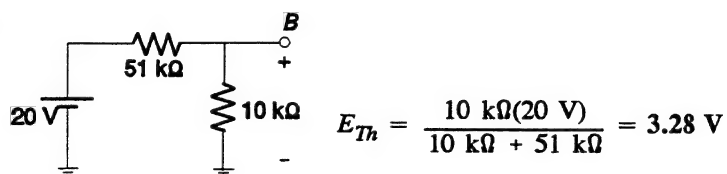

b.  $I_E R_E + V_{CE} + I_C R_C = 20 \text{ V}$   
 but  $I_C = I_E$   
 and  $I_E(R_C + R_E) + V_{CE} = 20 \text{ V}$   
 or  $I_E = \frac{20 \text{ V} - V_{CE}}{R_C + R_E} = \frac{20 \text{ V} - 8 \text{ V}}{2.2 \text{ k}\Omega + 0.5 \text{ k}\Omega} = \frac{12 \text{ V}}{2.7 \text{ k}\Omega} = 4.444 \text{ mA}$


c.

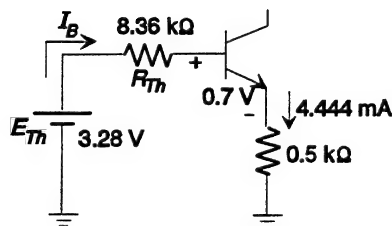

$E_{Th} - I_B R_{Th} - V_{BE} - V_E = 0$   
 and  $I_B = \frac{E_{Th} - V_{BE} - V_E}{R_{Th}} = \frac{3.28 \text{ V} - 0.7 \text{ V} - (4.444 \text{ mA})(0.5 \text{ k}\Omega)}{8.36 \text{ k}\Omega}$   
 $= \frac{2.58 \text{ V} - 2.222 \text{ V}}{8.36 \text{ k}\Omega} = \frac{0.358 \text{ V}}{8.36 \text{ k}\Omega} = 42.82 \mu\text{A}$

d.  $V_C = 20 \text{ V} - I_C R_C = 20 \text{ V} - (4.444 \text{ mA})(2.2 \text{ k}\Omega)$   
 $= 20 \text{ V} - 9.777 \text{ V}$   
 $= 10.223 \text{ V}$


14. (I)(a)  $R_N$ :

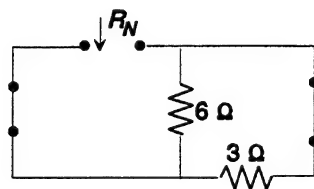


$R_N = 6 \Omega \parallel 3 \Omega = 2 \Omega$

$I_N$ :

$E_1$ :

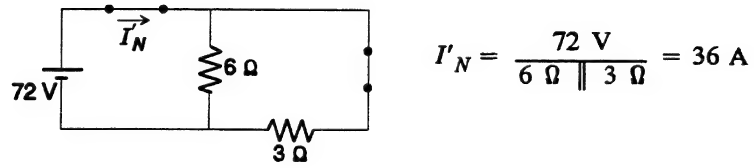


$E_2$ :

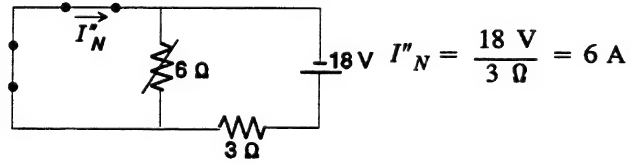

$$I_N = I'_N + I''_N = 36 \text{ A} + 6 \text{ A} = 42 \text{ A}$$


(II)(a)

$R_N$ :

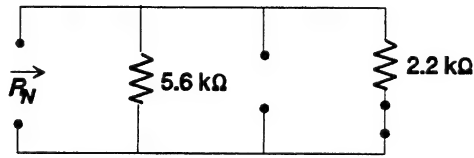


$I_N$ :

$I$ :

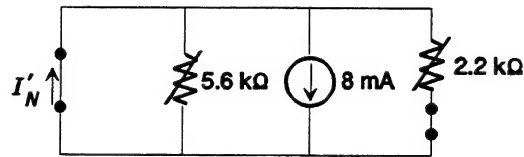


$E$ :

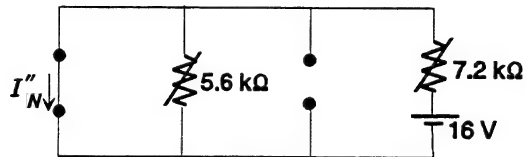




16. (I)(a)

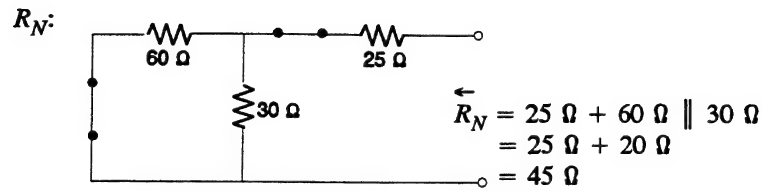

$I_N$ :

$E = 15 \, \text{V}$ :

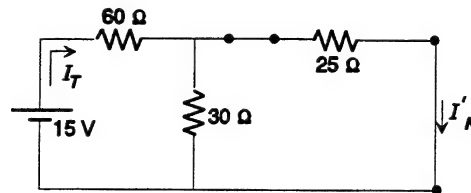


$$I_T = \frac{15 \, \text{V}}{60 \, \Omega + 30 \, \Omega \parallel 25 \, \Omega}$$

$$= 0.2037 \, \text{A}$$

$$I'_N = \frac{30 \, \Omega (I_T)}{30 \, \Omega + 25 \, \Omega}$$

$$= 0.1111 \, \text{A}$$

$E = 10 \, \text{V}$ :

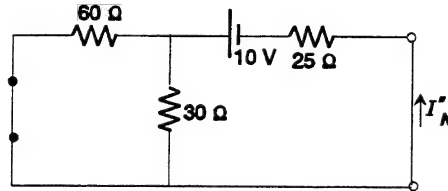

$$I''_N = \frac{10 \, \text{V}}{25 \, \Omega + 60 \, \Omega \parallel 30 \, \Omega}$$


$$= \frac{10 \, \text{V}}{25 \, \Omega + 20 \, \Omega}$$

$$= 0.2222 \, \text{A}$$

$$I_N (\text{dir of } I''_N) = I''_N - I'_N = 0.2222 \, \text{A} - 0.1111 \, \text{A} = 0.111 \, \text{A}$$


(II)(a)

$R_N$ :

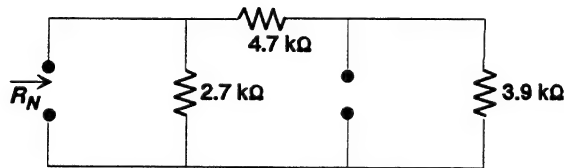


$$R_N = 2.7 \, \text{k}\Omega \parallel (4.7 \, \text{k}\Omega + 3.9 \, \text{k}\Omega) = 2.055 \, \text{k}\Omega$$

$I_N$ :

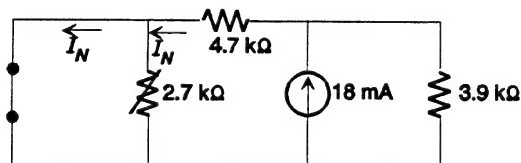


$$I_N = \frac{3.9 \, \text{k}\Omega (18 \, \text{mA})}{3.9 \, \text{k}\Omega + 4.7 \, \text{k}\Omega} = 8.163 \, \text{mA}$$


18. a.  $R_N$ :

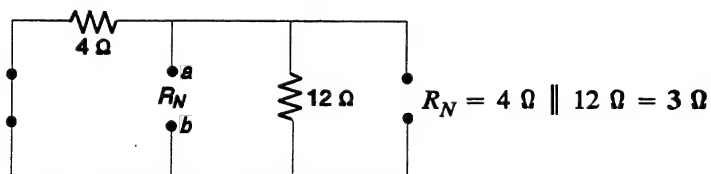

$E = 12\text{ V}$ :

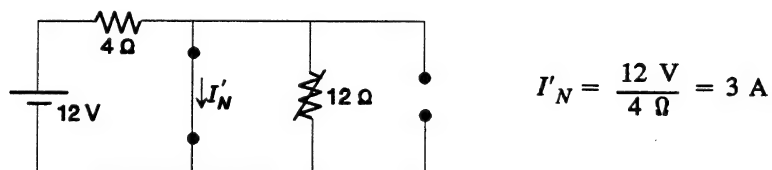


$I = 2\text{ A}$ :

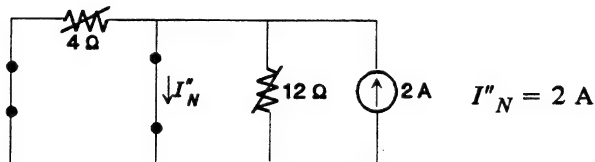


$$I_N = I'_N + I''_N = 3\text{ A} + 2\text{ A} = 5\text{ A}$$

b.  $R_N$ :


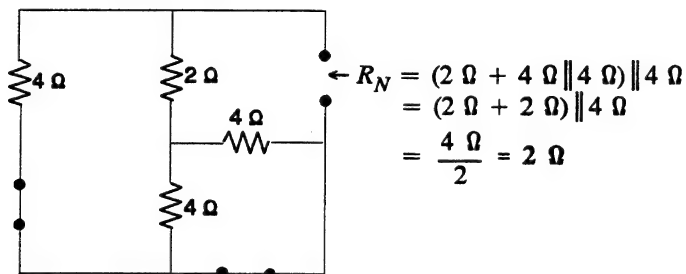


$I_N$ :

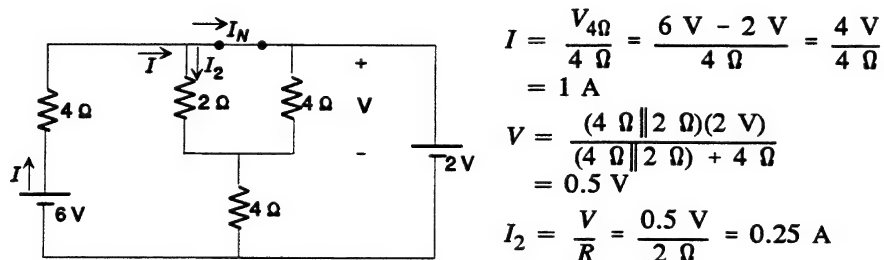


$$I_N = I - I_2 = 1\text{ A} - 0.25\text{ A} = 0.75\text{ A}$$

20. (I) a.

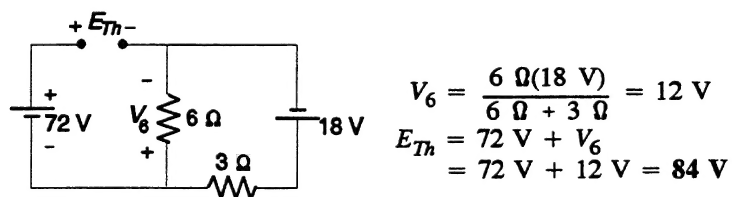
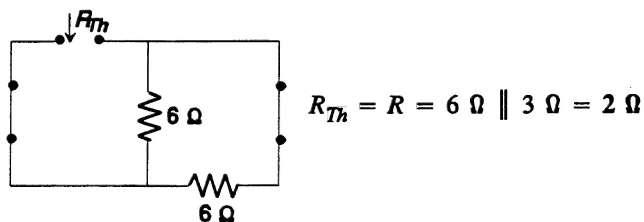


b.  $P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(84\ \text{V})^2}{4(2\ \Omega)} = 882\ \text{W}$

(II) a.  $R_{Th}$ :

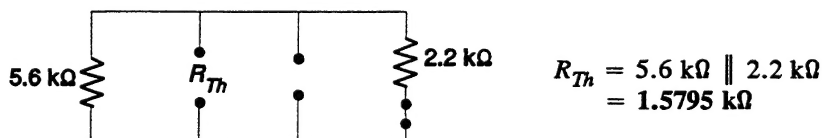


b.  $E_{Th}$ :

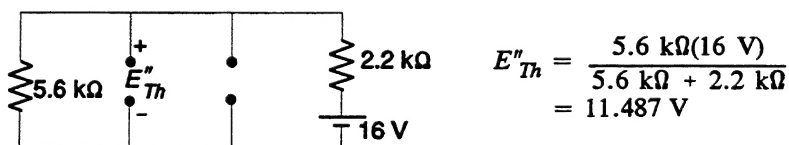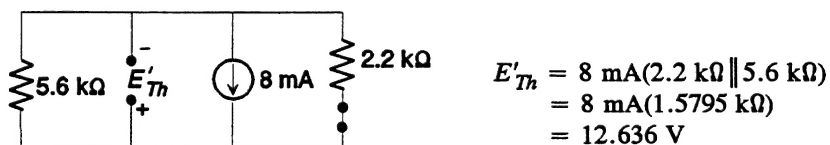


$E_{Th} \text{ (polarity of } E'_{Th}) = E'_{Th} - E''_{Th} = 12.636\ \text{V} - 11.487\ \text{V} = 1.149\ \text{V}$

$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(1.149\ \text{V})^2}{4(1.5795\ \text{k}\Omega)} = 0.21\ \text{mW}$



22. a.

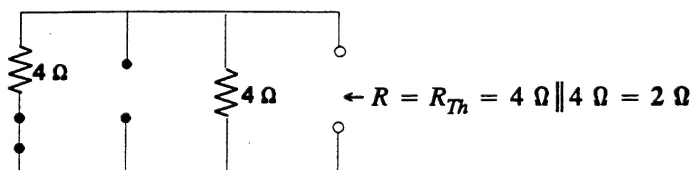


b.  $E_{Th}$ :

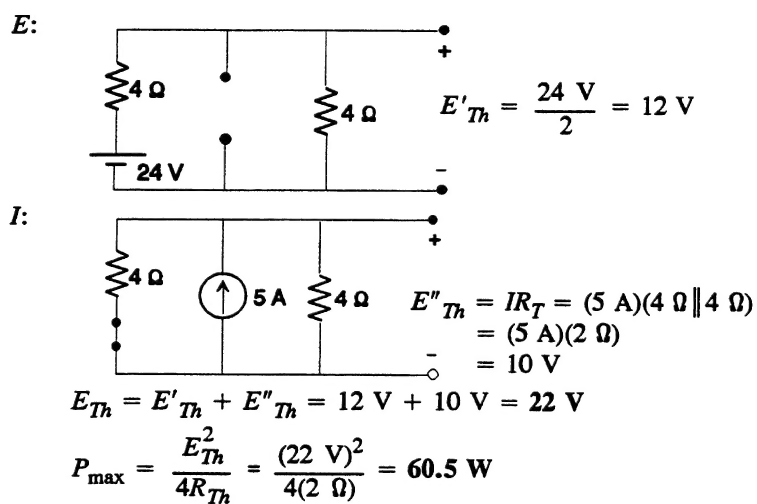


c.

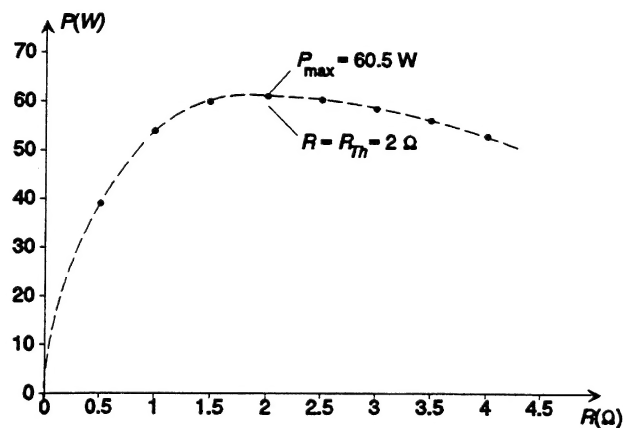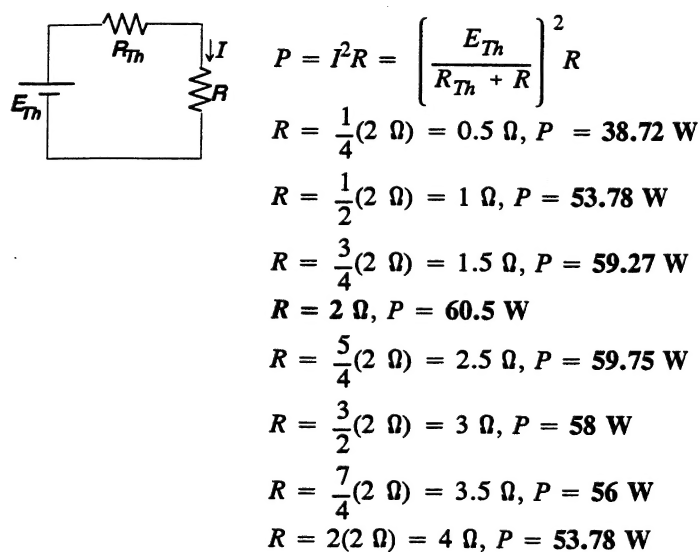

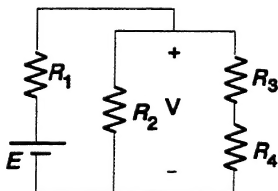24. a.  V, and therefore  $V_4$ , will be its largest value when  $R_2$  is as large as possible. Therefore choose  $R_2 = \text{open-circuit } (\infty \Omega)$ .


Then  $P_4 = \frac{V_4^2}{R_4}$  will be a maximum.

- b. No, examine each individually.

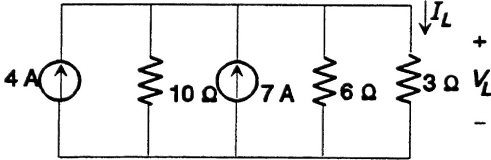26.  
$$\begin{aligned} I_T &= 4 \text{ A} + 7 \text{ A} = 11 \text{ A} \\ R_T &= 10 \Omega \parallel 6 \Omega \parallel 3 \Omega = 1.667 \Omega \\ V_L &= I_T R_T = (11 \text{ A})(1.667 \Omega) = 18.34 \text{ V} \\ I_L &= \frac{V_L}{R_L} = \frac{18.34 \text{ V}}{3 \Omega} = 6.113 \text{ A} \end{aligned}$$


28. 
$$\begin{aligned} I_T &= 2 \text{ A} - 0.2 \text{ A} - 0.001 \text{ A} = 1.799 \text{ A} \\ R_T &= 200 \Omega \parallel 200 \Omega \parallel 100 \Omega \parallel 10 \text{ k}\Omega = 49.751 \Omega \\ V_L &= I_T R_T = (1.799 \text{ A})(49.751 \Omega) = 89.5 \text{ V} \\ I_L &= \frac{V_L}{R_L} = \frac{89.5 \text{ V}}{200 \Omega} = 0.448 \text{ A} \end{aligned}$$

30. 
$$\begin{aligned} I_{eq} &= \frac{(4 \text{ mA})(8.2 \text{ k}\Omega) + (8 \text{ mA})(4.7 \text{ k}\Omega) - (10 \text{ mA})(2 \text{ k}\Omega)}{8.2 \text{ k}\Omega + 4.7 \text{ k}\Omega + 2 \text{ k}\Omega} \\ &= \frac{32.8 \text{ V} + 37.6 \text{ V} - 20 \text{ V}}{14.9 \text{ k}\Omega} = 3.3826 \text{ mA} \\ R_{eq} &= 8.2 \text{ k}\Omega + 4.7 \text{ k}\Omega + 2 \text{ k}\Omega = 14.9 \text{ k}\Omega \\ I_L &= \frac{R_{eq} I_{eq}}{R_{eq} + R_L} = \frac{(14.9 \text{ k}\Omega)(3.3826 \text{ mA})}{14.9 \text{ k}\Omega + 6.8 \text{ k}\Omega} = 2.3226 \text{ mA} \\ V_L &= I_L R_L = (2.3226 \text{ mA})(6.8 \text{ k}\Omega) = 15.7937 \text{ V} \end{aligned}$$

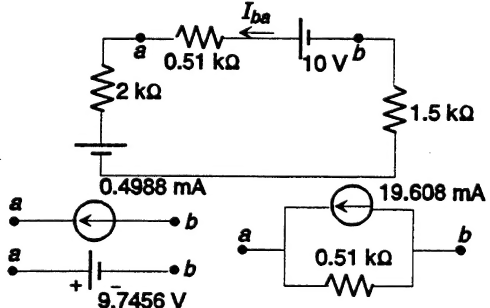32.  
$$\begin{aligned} I_{ba} &= \frac{10 \text{ V} - 8 \text{ V}}{2 \text{ k}\Omega + 0.51 \text{ k}\Omega + 1.5 \text{ k}\Omega} \\ &= 0.4988 \text{ mA} \\ V_{0.51 \text{ k}\Omega} &= (0.4988 \text{ mA})(0.51 \text{ k}\Omega) \\ &= 0.2544 \text{ V} \\ V_{ab} &= 10 \text{ V} - 0.2544 \text{ V} = 9.7456 \text{ V} \end{aligned}$$

34. a. 
$$I_s = \frac{24 \text{ V}}{8 \text{ k}\Omega + \frac{24 \text{ k}\Omega}{3}} = 1.5 \text{ mA}, I = \frac{I_s}{3} = 0.5 \text{ mA}$$

b.

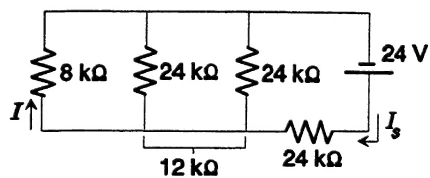

$$I_s = \frac{24 \text{ V}}{24 \text{ k}\Omega + 8 \text{ k}\Omega \parallel 12 \text{ k}\Omega} = 0.8333 \text{ mA}$$

$$I = \frac{12 \text{ k}\Omega(I_s)}{12 \text{ k}\Omega + 8 \text{ k}\Omega} = 0.5 \text{ mA}$$

c. yes

36. a. 
$$I_{R_2} = \frac{R_1(I)}{R_1 + R_2 + R_3} = \frac{3\Omega(6 \text{ A})}{3 \Omega + 2 \Omega + 4 \Omega} = 2 \text{ A}$$
  

$$V = I_{R_2}R_2 = (2 \text{ A})(2 \Omega) = 4 \text{ V}$$

b. 
$$I_{R_1} = \frac{R_2(I)}{R_1 + R_2 + R_3} = \frac{2 \Omega(6 \text{ A})}{3 \Omega + 2 \Omega + 4 \Omega} = 1.333 \text{ A}$$
  

$$V = I_{R_1}R_1 = (1.333 \text{ A})(3 \Omega) = 4 \text{ V}$$

c. yes